

CS 261

Fall 2016

Mike Lam, Professor

Sequential Circuits

Circuits

- **Circuits** are formed by linking gates together
 - Inputs and outputs
 - Link output of one gate to input of another
 - Some gates have multiple inputs and/or outputs
 - **Combinational** circuits: outputs are a boolean function of inputs
 - Not time-dependent
 - Used for computation
 - **Sequential** circuits: output is dependent on previous inputs
 - Time-dependent
 - Used for memory


Circuit memory

- Question: How do we make a circuit “remember” something?






Circuit memory

- Question: How do we make a circuit “remember” something?
 - Answer: Create a feedback loop!
 - Creates a “storage” circuit, often called a **latch**
 - Instead of truth table, draw a **timing diagram**
 - Shows how input/output signals change with respect to time
 - Given input signals in diagram, we can determine output signals





SR AND-OR latch

 

S = "set" R = "reset"

    
 


SR NOR latch

   
 


Disallow $S=1, R=1$ because $Q' \neq !Q$

D latch

  


From "Code" book: S = "Save that bit!"

  


Signal changes

 - **Edge-triggered** latches change Q on **rising** edge of “set” signal
- **Master-slave** latches change Q on **falling** edge of “set” signal






Original (edge-triggered) D latch

 

Master-slave D latch

Master-slave D latch

Original D latch:

   

Clocks

- Provide oscillating signal
- Often used as “set” signal for latches
- Keep computation and memory in sync
- Clocked latches are called **flip-flops**




Flip-flop types

- **SR**: “set-reset”
- **D**: “data” bit + clock
- **T**: “toggle”
- **JK**: like SR + T (toggle when $S=1, R=1$)
 - J is S, K is R
- Any of these can be used to build the others
- Also can be built from basic logic gates in multiple ways


Registers

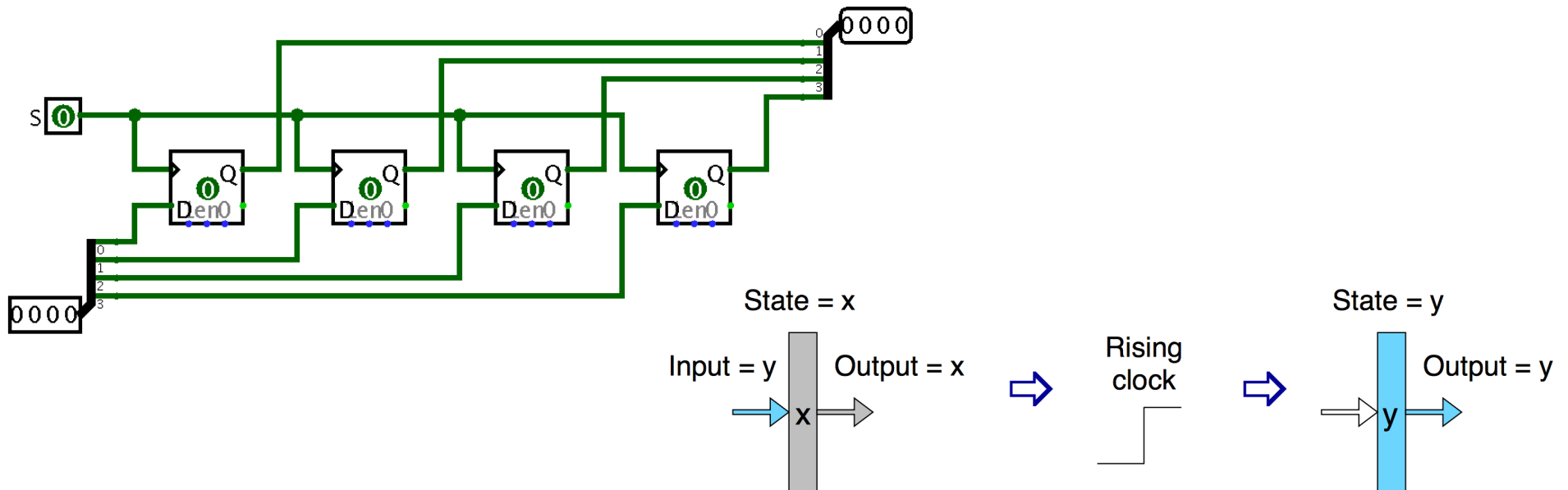- **Registers**: arrays of flip-flops with a single set/clock input
- Connected by **buses** (groups of wires) to other components
- Edge triggering allows computation to stabilize before results are saved
- Caveat: difference between **hardware** registers and **program** registers
 - Former are physical, latter are logical (and stored in a **register file**)



Register files

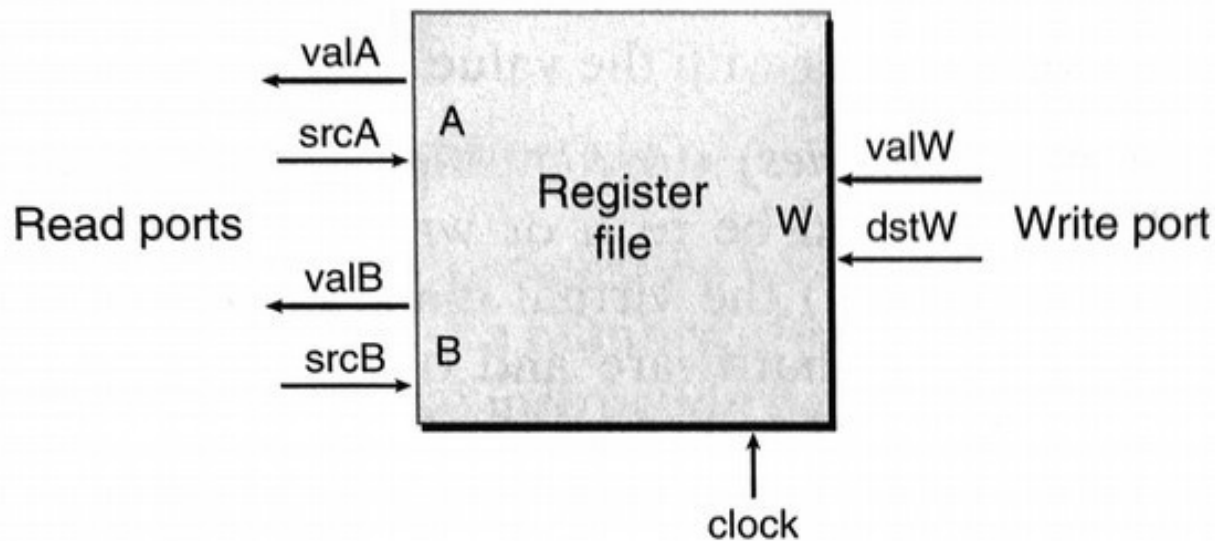
- **Register files**: multiple registers w/ selector inputs
 - Use multiplexors to differentiate




Use multiplexors to read/write from the appropriate register using `srcA`, `srcB`, or `dstW` signals (set `dstW` to `0xF` to read only)

Memory

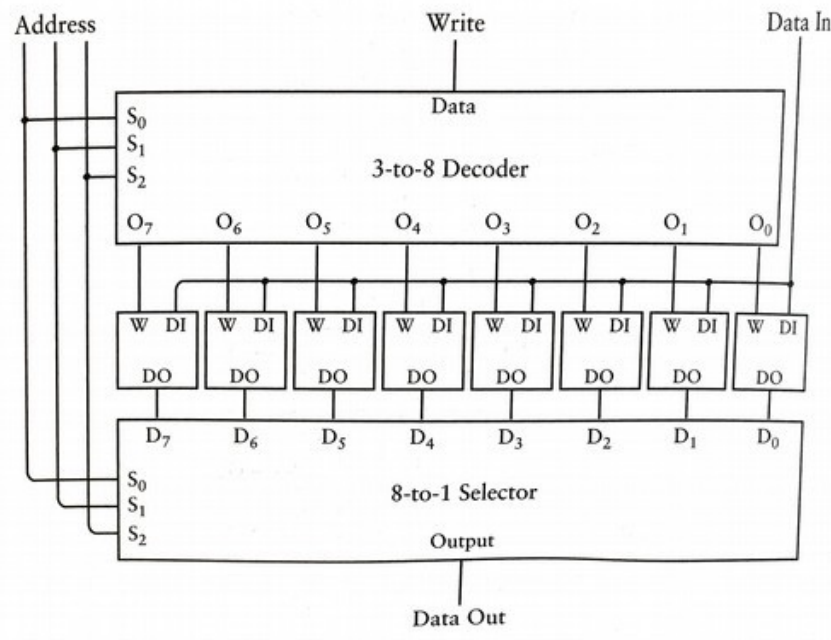- Memory: multiple flip-flops w/ address input
 - **Random access memory** (RAM) - can access any address at any time
 - Use decoder (translates 3-bit number to 8 “set” signals) to write data
 - Use selector (multiplexor) to read data




Single RAM array

 

Abstraction of multiple RAM arrays

Shift registers

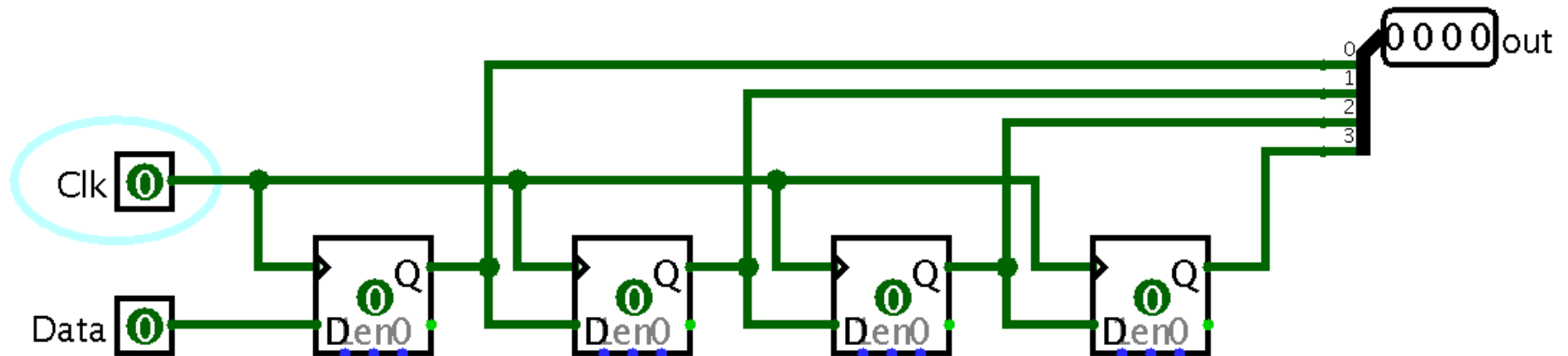- Uses chained flip-flops to perform **bit shifts**
 - Left vs. right shift
 - Serial-in vs. parallel-in



Counters

- Uses rippled flip-flops w/ feedback to **count**
 - Similar to adders

