

CS 261

Fall 2017

Mike Lam, Professor

Sequential Circuits

Circuits

- **Circuits** are formed by linking gates together
 - Inputs and outputs
 - Link output of one gate to input of another
 - Some gates have multiple inputs and/or outputs
 - **Combinational** circuits: outputs are a boolean function of inputs
 - Not time-dependent
 - Used for computation
 - **Sequential** circuits: output is dependent on previous outputs
 - Time-dependent
 - Used for memory


Circuit memory

- Question: How do we make a circuit “remember” something?






Circuit memory

- Question: How do we make a circuit “remember” something?
 - Answer: Create a feedback loop!
 - Creates a “storage” circuit, often called a **latch**
 - Truth table must include previous state
 - Alternatively, draw a **timing diagram**
 - Shows how input/output signals change with respect to time
 - Given input signals in diagram, we can determine output signals





SR AND-OR latch

 

S = "set" R = "reset"

    
 


SR NOR latch

   
 


Disallow $S=1, R=1$ because $Q' \neq !Q$

D latch

  


From "Code" book: S = "Save that bit!"

  


Signal changes

 - The original D latch reflects D input on Q as long as “set” is on
- **Edge-triggered** latches change Q on **rising** edge of “set” signal
- **Master-slave** latches change Q on **falling** edge of “set” signal







Edge-triggered D latch

 

Master-slave D latch


Master-slave D latch

Original D latch:

    

Clocks

 - Provide oscillating signal
- Often used as “set” signal for latches
- Keeps computation and memory in sync
- Clocked latches are called **flip-flops**
- The clock period is the inverse of the frequency (measured in *hertz*)
- The length of a clock period determines the minimum time an instruction takes to execute





Flip-flop types

- **SR**: “set-reset”
- **D**: “data” bit + clock
- **T**: “toggle”
- **JK**: like SR + T (toggle when $S=1, R=1$)
 - J is S, K is R
- Any of these can be used to build the others
- Also can be built from basic logic gates in multiple ways


Registers

  - **Registers**: arrays of flip-flops with a single set/clock input
- Connected by **buses** (groups of wires) to other components
- Edge triggering allows computation to stabilize before results are saved
- Caveat: difference between **hardware** registers and **program** registers
 - Former are physical, latter are logical (and stored in a **register file**)



Register files

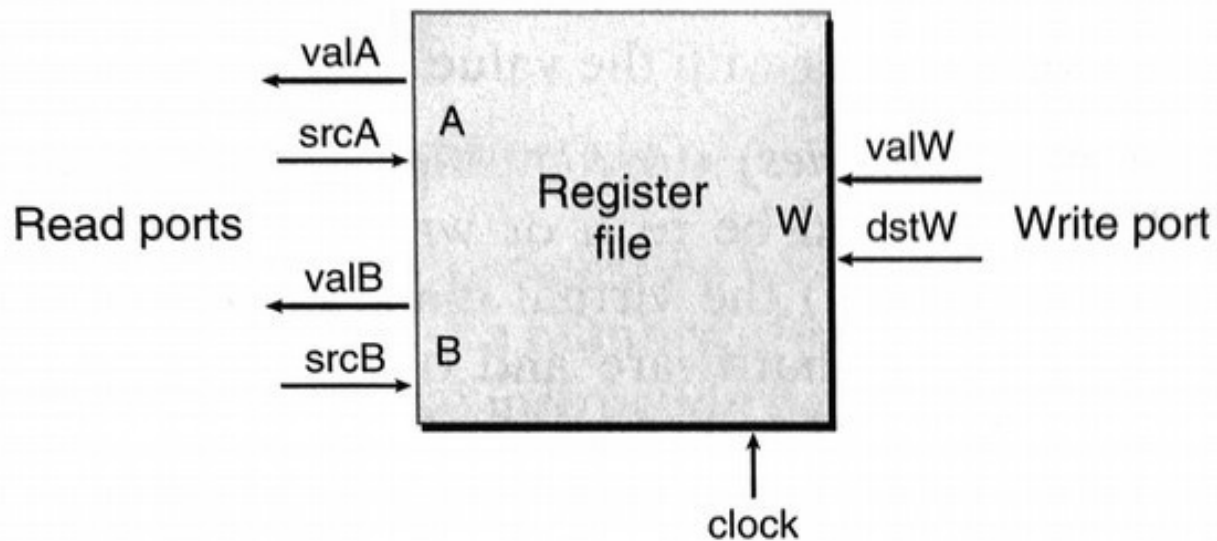
- **Register files**: multiple registers w/ selector inputs
 - Use multiplexors to differentiate




Use multiplexors to read/write from the appropriate register using srcA, srcB, or dstW signals (set dstW to 0xF to read only)

Memory

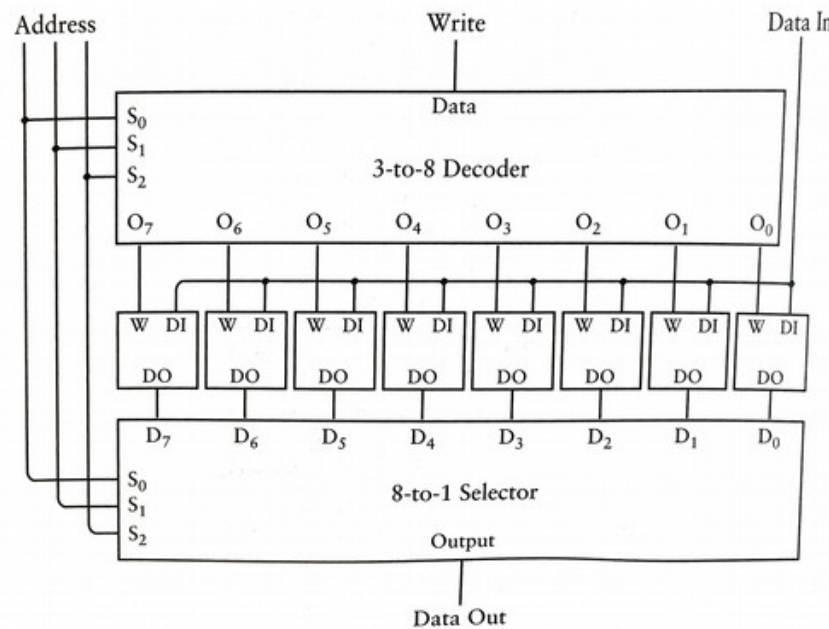- Memory: multiple flip-flops w/ address input
 - **Random access memory** (RAM) - can access any address at any time
 - Use decoder (translates 3-bit number to 8 “set” signals) to write data
 - Use selector (multiplexor) to read data




Single RAM array

 


Abstraction of multiple RAM arrays

ALUs and memory

 - Combine **adders** and **multiplexors** to make **arithmetic/logic units**
- Combine **flip-flops** to make **register files** and **main memory**



Basic Arithmetic Logic Unit (ALU)

 

CPUs

- Combine **ALU** with **registers** and **memory** to make CPUs

