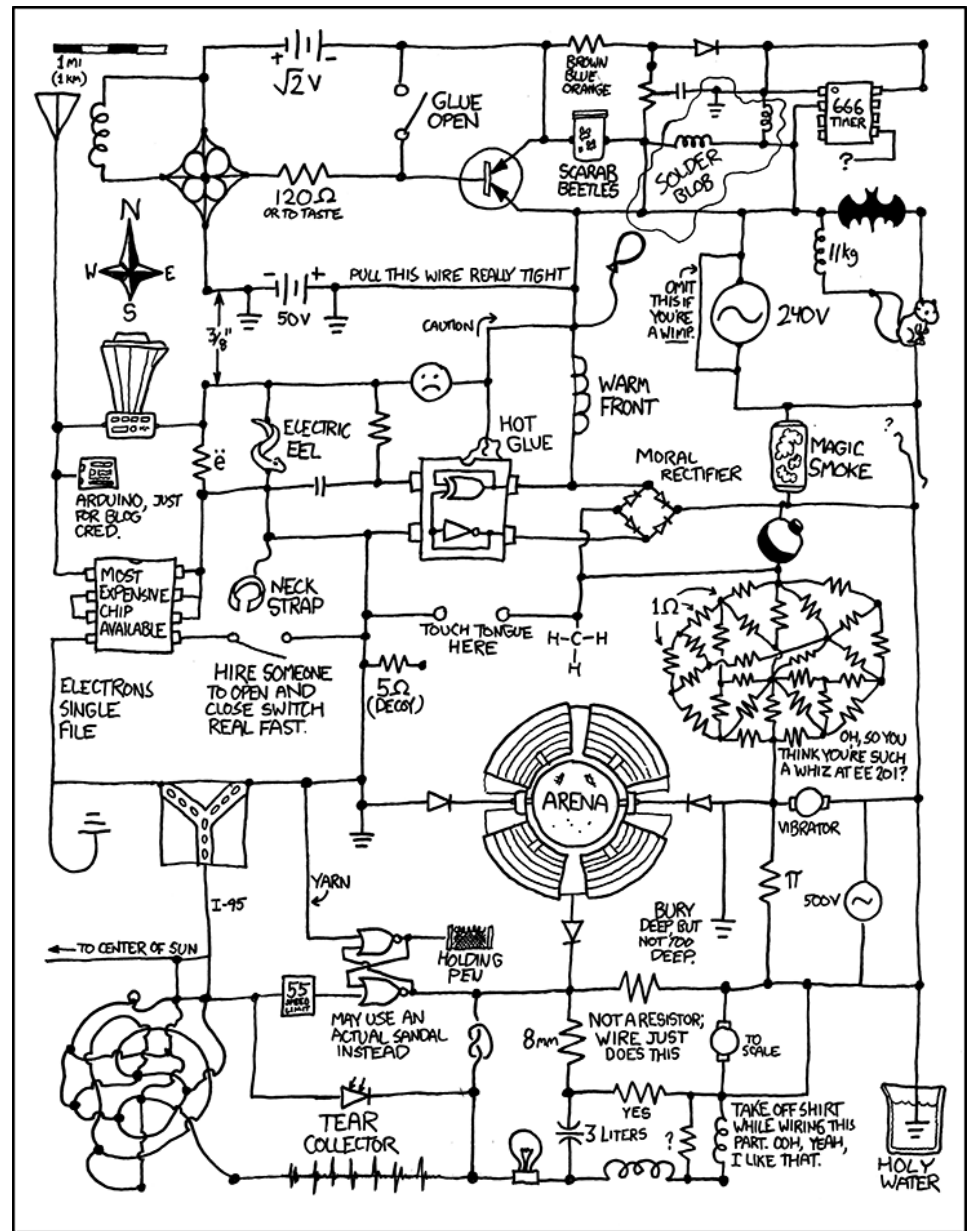


# CS 261 Fall 2018

Mike Lam, Professor




## Combinational Circuits

# The final frontier

- Java programs running on Java VM
- C programs compiled on Linux
- Assembly / machine code on CPU + memory
- ???
- Switches and electric signals

# Aside: Relays

- From “Code” recommended reading:

 


Relay

Light is on when switch is on


*Question: what happens if we connect the light bulb to the other contact?*

# Aside: Relays

- From “Code” recommended reading:

 


Regular relay

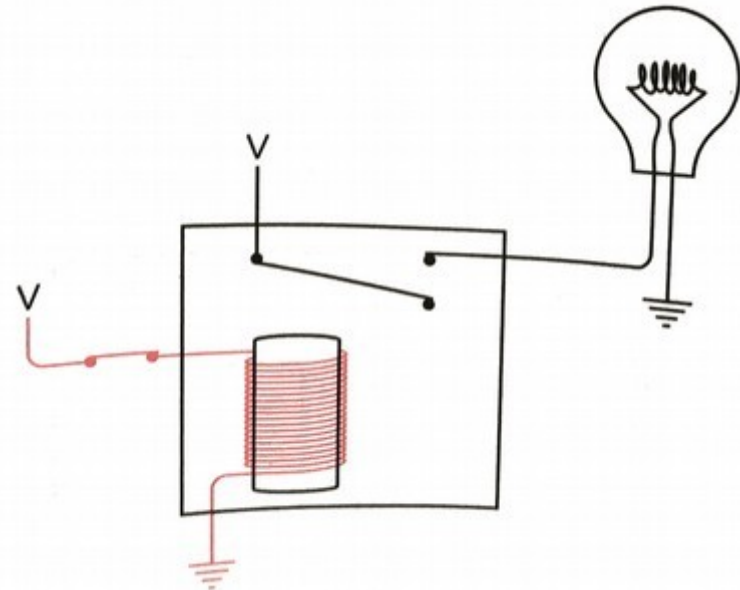


Inverted relay (NOT)

# Aside: Relays

- From “Code” recommended reading:

 



Relays in series (AND)

 


Relays in parallel (OR)
  
# Digital hardware

- Digital signals are transmitted via electric signals by varying voltages
  - 1.0 V (high) = binary 1
  - 0.0 V (low) = binary 0
  - Use a threshold to distinguish





AND

 

OR
  
# Transistors

- **Transistors** are the fundamental hardware component of computing
  - Similar to relays; replaced vacuum tubes
    - Smaller, more reliable, and use less energy
    - Primary functions: switching and amplification
  - Mostly silicon-based semiconductors now
    - **Metal–Oxide–Semiconductor Field-Effect Transistor** (MOSFET)
    - n-channel (“on” when  $V_{\text{gate}} = 1\text{V}$ ) vs. p-channel (“off” when  $V_{\text{gate}} = 1\text{V}$ )
    - Mass-produced on **integrated circuit** chips
  - For convenience, we abstract their behavior using **logic gates**



# Logic gates

- Primary gates:



&	0	1
0	0	0
1	0	1

AND



	0	1
0	0	1
1	1	1

OR



!	
0	1
1	0

NOT



	0	1
0	1	1
1	1	0

NAND



	0	1
0	1	0
1	0	0

NOR



^	0	1
0	0	1
1	1	0

XOR



# Lab

- Part 1

# Important properties


- Identity:  $a \text{ AND } 1 = a$        $(a \text{ OR } 0) = a$
  - Constants:  $a \text{ AND } 0 = 0$        $(a \text{ OR } 1) = 1$ 
    - Also:  $a \text{ NAND } 0 = 1$        $(a \text{ NOR } 1) = 0$
  - Inverses:  $a \text{ NAND } 1 = !a$        $(a \text{ NOR } 0) = !a$ 
    - Also:  $a \text{ NAND } a = !a$        $a \text{ NOR } a = !a$
  - Double inverse:  $!!a = a$ 
    - Or:  $\text{NOT}(\text{NOT}(a)) = a$
  - De Morgan's law:  $!(a \ \& \ b) = !a \ | \ !b$ 
    - Alternatively:  $!(a \ | \ b) = !a \ \& \ !b$
- (remember this from CS 227?)*

# Basic circuits

- **Circuits** are formed by connecting gates together
  - Inputs and outputs
    - Link output of one gate to input of another
    - Some circuits have multiple inputs and/or outputs
  - Textbook uses Hardware Description Language (HDL)
  - Equivalent to **boolean formulas** or **functions**
    - $f(g(x, y))$  means “apply  $f$  to the result of applying  $g$  to  $x$  and  $y$ ”
    - In a diagram:  $x, y \rightarrow g \rightarrow f$  (i.e., ordering is  $g$  first, then  $f$ )

 
# Basic circuits

- $f(g(x, y))$  means “apply  $f$  to the result of applying  $g$  to  $x$  and  $y$ ”
  - In a diagram:  $x, y \rightarrow g \rightarrow f$  (i.e., ordering is  $g$  first, then  $f$ )
- NAND example: (similarly for NOR)
  - Infix/boolean notation:  $a \text{ NAND } b = \neg(a \ \& \ b)$
  - Function notation:  $\text{NAND}(a, b) = \text{NOT}(\text{AND}(a, b))$


 
# Basic circuits

- $f(g(x, y))$  means “apply  $f$  to the result of applying  $g$  to  $x$  and  $y$ ”
  - In a diagram:  $x, y \rightarrow g \rightarrow f$  (i.e., ordering is  $g$  first, then  $f$ )
- NAND example: (similarly for NOR)
  - Infix/boolean notation:  $a \text{ NAND } b = \neg(a \ \& \ b)$
  - Function notation:  $\text{NAND}(a, b) = \text{NOT}(\text{AND}(a, b))$



	0	1
0	0	0
1	0	1

a AND b

	0	1
0	1	1
1	1	0



	0	1
0	1	1
1	1	0

a NAND b


# Basic circuits

- Circuits are **equivalent** if the truth tables are the same
  - $a \text{ XOR } b = (a \text{ OR } b) \text{ AND } (a \text{ NAND } b)$
  - $\text{XOR}(a, b) = \text{AND}(\text{OR}(a,b), \text{NAND}(a,b))$



$\wedge$	0	1
0	0	1
1	1	0

XOR

 


# Basic circuits

- Circuits are **equivalent** if the truth tables are the same
  - $a \text{ XOR } b = (a \text{ OR } b) \text{ AND } (a \text{ NAND } b)$
  - $\text{XOR}(a, b) = \text{AND}(\text{OR}(a,b), \text{NAND}(a,b))$



$\wedge$	0	1
0	0	1
1	1	0

XOR

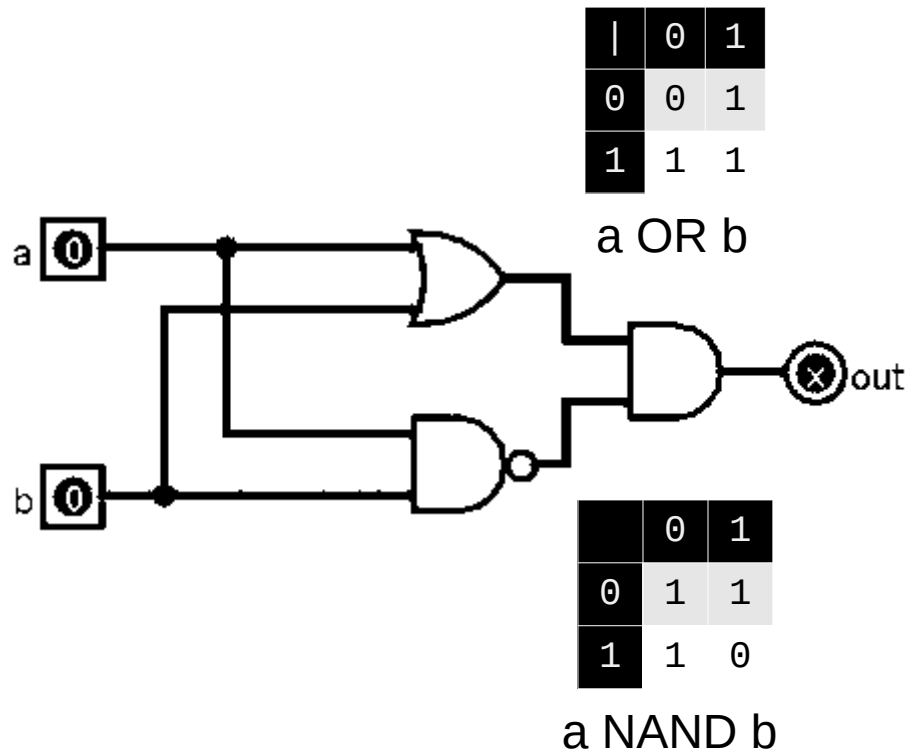


# Basic circuits

- Circuits are **equivalent** if the truth tables are the same
  - $a \text{ XOR } b = (a \text{ OR } b) \text{ AND } (a \text{ NAND } b)$
  - $\text{XOR}(a, b) = \text{AND}(\text{OR}(a,b), \text{NAND}(a,b))$



$\wedge$	0	1
0	0	1
1	1	0

XOR

 

	0	1
0	0	1
1	1	0

(a OR b) AND  
(a NAND b)



# Basic circuits


- Circuits are **equivalent** if the truth tables are the same
  - $a \text{ XOR } b = (a \text{ OR } b) \text{ AND } (a \text{ NAND } b)$
  - $\text{XOR}(a, b) = \text{AND}(\text{OR}(a,b), \text{NAND}(a,b))$

a	b	$a \wedge b$	$f(a, b)$
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0



$\wedge$	0	1
0	0	1
1	1	0

XOR

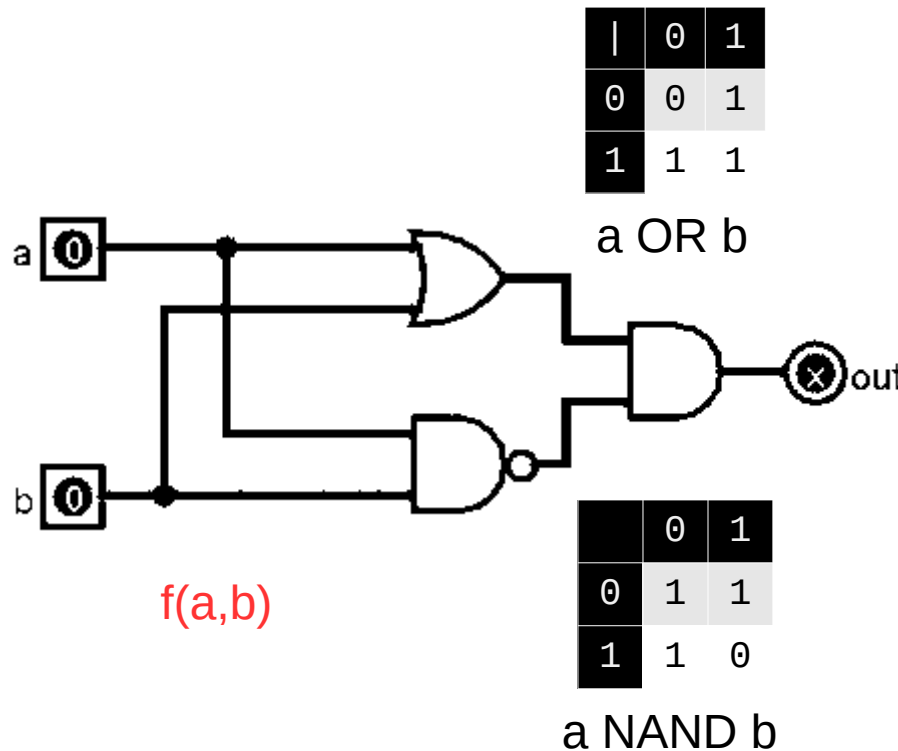

	0	1
0	0	1
1	1	1

$a \text{ OR } b$

	0	1
0	1	1
1	1	0

$a \text{ NAND } b$

	0	1
0	0	1
1	1	0


$(a \text{ OR } b) \text{ AND } (a \text{ NAND } b)$

# Lab

- Part 2
 
# Universal gates

- NAND and NOR gates are **universal**
  - Each one alone can reproduce all other gates
  - Example:  **$a \text{ AND } b = a \& b = \neg(\neg(a \& b)) = \neg(a \text{ NAND } b) = (a \text{ NAND } b) \text{ NAND } (a \text{ NAND } b)$**



	0	1
0	1	1
1	1	0

a NAND b

	0	1
0	0	0
1	0	1


(a NAND b) NAND  
(a NAND b)

	0	1
0	0	0
1	0	1

a AND b
 
# Universal gates

- NAND and NOR gates are **universal**
  - Each one alone can reproduce all other gates
  - Example: **a AND b** =  $a \& b = \neg(\neg(a \& b)) = \neg(a \text{ NAND } b)$   
= **(a NAND b) NAND (a NAND b)**
    - Similarly: **a AND b** =  $\neg(\neg(a \& b)) = \neg(\neg a \mid \neg b) = \neg a \text{ NOR } \neg b =$   
**(a NOR a) NOR (b NOR b)**



	0	1
0	1	1
1	1	0

a NAND b


	0	1
0	0	0
1	0	1

(a NAND b) NAND  
(a NAND b)



	0	1
0	0	0
1	0	1

a AND b

 

(a NOR a) NOR  
(b NOR b)


# Circuit types

- Two main kinds of circuits:
  - **Combinational** circuits: outputs are a boolean function of inputs
    - Not time-dependent
    - Used for **computation**
  - **Sequential** circuits: output is dependent on previous outputs
    - Time-dependent
    - Used for **memory**

# Computation


- Goal: identify circuits that perform useful computation
  - Testing bits to see if they're equal
  - Selecting between multiple inputs
  - Adding or subtracting bits
  - Bitwise operations (AND, OR, XOR)
  - Make them work on bytes instead of bits

# Equality

 

$$a \text{ EQ } b = (a \ \& \ b) \ | \ (!a \ \& \ !b)$$


# Multiplexor (“selector”)

 

$$\text{MUX}(a, b, s) = (s \ \& \ a) \ | \ (!s \ \& \ b)$$




# Half adders

 

Half Adder

A	B	C	S
0	0	?	?
0	1	?	?
1	0	?	?
1	1	?	?

# Half adders

 

Half Adder

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


$$a + b = a \wedge b + a \& b$$

sum          carry

# Abstraction

- Name circuits, then use them to build more complex circuits
  - E.g., use bit-level EQ to build a word-level equality circuit:

**A). Bit-level implementation**

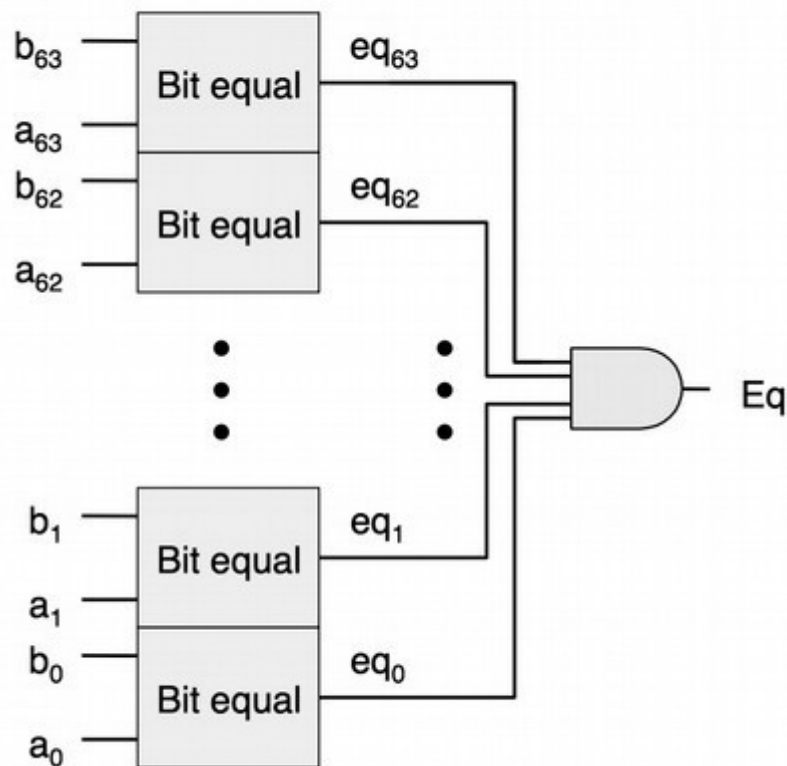


**B). Word-level abstraction**




# Word-level 2-way multiplexer


**A). Bit-level implementation**

 

**B). Word-level abstraction**

 


# Word-level 4-way multiplexer

 

How many selector inputs would be required for eight data inputs?


How many data inputs could be supported using four selector inputs?

# Full adders

 


Full Adder

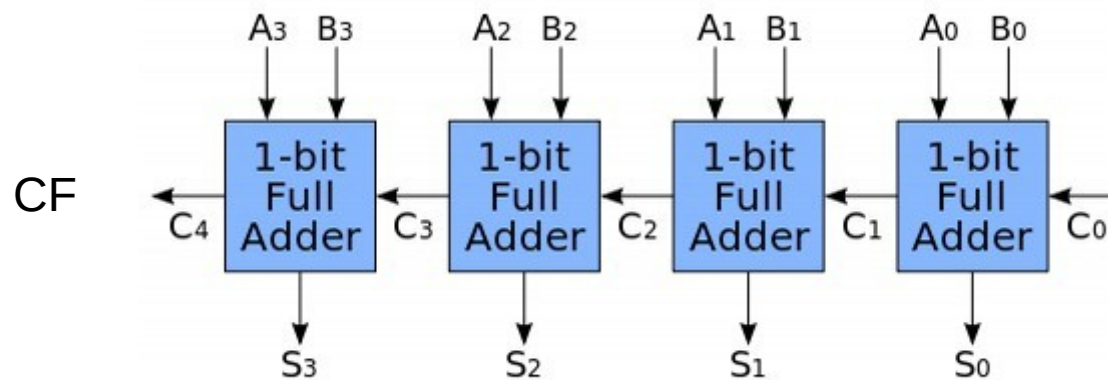Connect full adders to build a **ripple-carry adder** that can handle multi-bit addition:




# Adder/subtractor

 


In two's complement:  $B - A = B + !A + 1$
 
# ALUs and memory

- Combine **adders** and **multiplexors** to make **arithmetic/logic units**
- Combine **flip-flops** to make **register files** and **memory**




Basic Arithmetic Logic Unit (ALU)

 



 
# CPUs

- Combine **ALU** with **registers** and **memory** to make CPUs


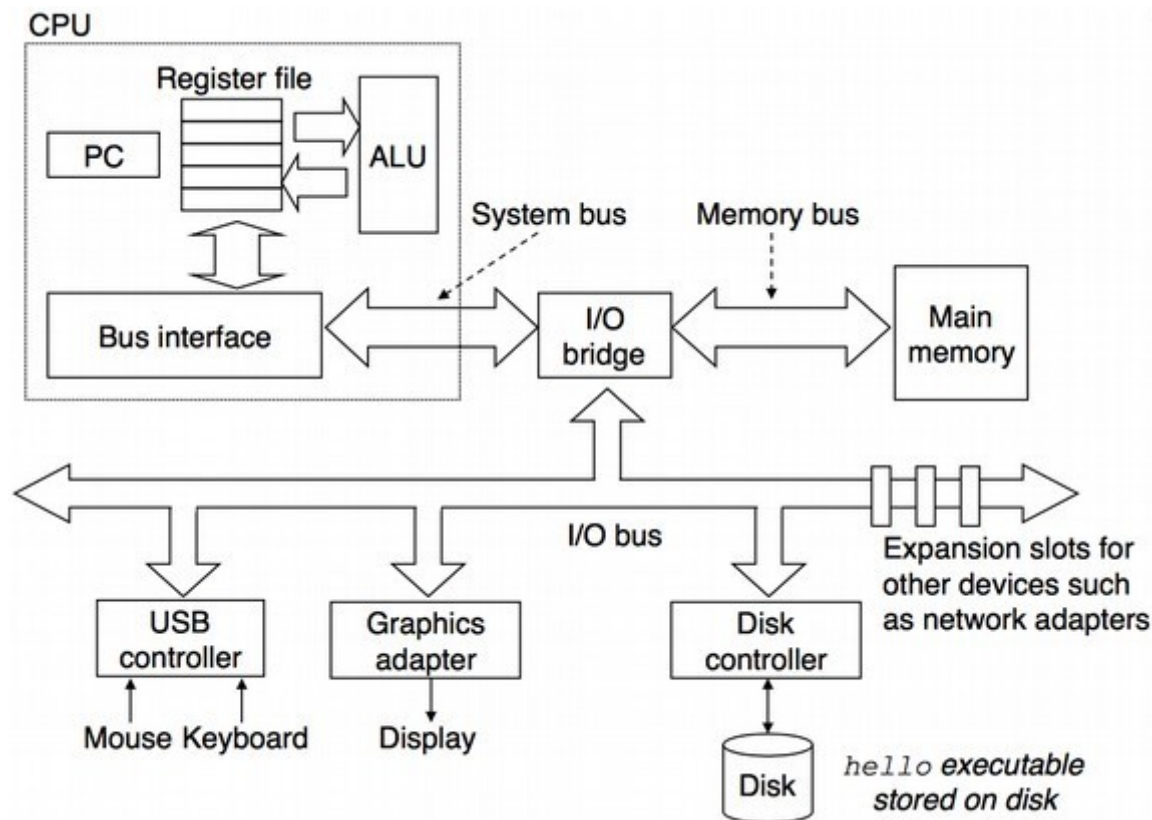
# Computers

- Combine **CPU** with other electronic components and devices (similarly constructed) communicating via **buses** to make a **computer**



# Big picture

- Basic systems design approach: exploit **abstraction**
  - Start with simple components
  - Combine to make more complex components
  - Repeat using the new components as **black box** “simple components”
- This is true of most areas in systems
  - **CS 261**: transistors → gates → circuits → adders/flip-flops → ALUs/registers → CPUs/memory → computers
  - **CS 261**: machine code → assembly → C code → Java/Python code
  - **CS 361/470**: threads → processes → nodes → networks/clusters
  - **CS 432**: scanner → parser → analyzer → code generator → optimizer
  - **CS 450**: files + processes + I/O → kernel → operating system

# Course status

- We've hit the bottom
  - Or at least as far down as we're going to go (logic gates); from here we go back up!
- Next week
  - Sequential circuits
  - CPU architecture

Suggestion: download **Logisim** (already installed on lab machines) and play around with some circuits!

# Lab

- Part 3