

CS 261

Fall 2022


Mike Lam, Professor

THIS IS WHAT LEARNING LOGIC GATES FEELS LIKE

SEE, YOU JUST CONNECT THIS 12 INPUT REVERSE FLIP-FLOP TO THE CONTROLLED TWO-THIRDS ADDER, WHICH RESETS THE LATCHES IN THE NOT-NAND RELAY ARRAY, THEN LOOP BACK TO ODD-NUMBER INPUTS AND REVERSE ALL YOUR SWITCHES!

AND WHAT'S THAT DO?

SUBTRACTION.

 

<http://smbc-comics.com/comic/logic-gates>


Combinational Circuits

The final frontier

- Java programs running on Java VM
 - Or Python programs running in Python interpreter
- C programs compiled on Linux
- Assembly / machine code on CPU + memory
- ???
- Electricity?


Aside: Relays

- From “Code” recommended reading:

 

Relay (off)

Light is on when switch is on

 


Relay (on)


Question: what happens if we connect the light bulb to the other contact?

Aside: Relays

- From “Code” recommended reading:

 


Regular relay

 


Inverted relay (NOT)

Aside: Relays

- From “Code” recommended reading:

 



Relays in series (AND)

 


Relays in parallel (OR)

Digital hardware

  - Digital signals are transmitted via electric signals by varying voltages
 - 1.0 V (high) = binary 1
 - 0.0 V (low) = binary 0
 - Use a threshold to distinguish





AND

 

OR

Transistors

- **Transistors** are the fundamental hardware component of computing
 - Similar to relays; replaced vacuum tubes
 - Smaller, more reliable, and use less energy
 - Primary functions: switching and amplification
 - Mostly silicon-based semiconductors now
 - **Metal–Oxide–Semiconductor Field-Effect Transistor** (MOSFET)
 - n-channel (“on” when $V_{\text{gate}} = 1\text{V}$) vs. p-channel (“off” when $V_{\text{gate}} = 1\text{V}$)
 - Mass-produced on **integrated circuit** chips
 - For convenience, we abstract their behavior using **logic gates**

  

Logic gates

- Primary gates:



&	0	1
0	0	0
1	0	1

AND



	0	1
0	0	1
1	1	1

OR



!	
0	1
1	0

NOT



	0	1
0	1	1
1	1	0

NAND



	0	1
0	1	0
1	0	0

NOR








^	0	1
0	0	1
1	1	0

XOR

Fluid-based gate visualization

     - <https://i.imgur.com/wUhtCgL.gifv>
- <https://i.imgur.com/UJyNd9T.gifv>




Basic circuits

- **Circuits** are formed by connecting gates together
 - Inputs and outputs
 - Link output of one gate to input of another
 - Some circuits have multiple inputs and/or outputs
 - Textbook uses Hardware Description Language (HDL)
 - Equivalent to **boolean formulas** or **functions**
 - $f(g(x, y))$ means “apply f to the result of applying g to x and y ”
 - In a diagram: $x, y \rightarrow g \rightarrow f$ (i.e., ordering is g first, then f)

Basic circuits

 - $f(g(x, y))$ means “apply f to the result of applying g to x and y ”
 - In a diagram: $x, y \rightarrow g \rightarrow f$ (i.e., ordering is g first, then f)
- NAND example: (similarly for NOR)
 - Infix/boolean notation: $a \text{ NAND } b = \text{NOT}(a \text{ AND } b) = !(a \ \& \ B)$
 - Function notation: $\text{NAND}(a, b) = \text{NOT}(\text{AND}(a, b))$



&	0	1
0	0	0
1	0	1

a AND b

	0	1
0	1	1
1	1	0



	0	1
0	1	1
1	1	0

a NAND b


Basic circuits

- Circuits are **equivalent** if the truth tables are the same
 - $a \text{ XOR } b = (a \text{ OR } b) \text{ AND } (a \text{ NAND } b)$
 - $\text{XOR}(a, b) = \text{AND}(\text{OR}(a,b), \text{NAND}(a,b))$



\wedge	0	1
0	0	1
1	1	0

XOR

 


Basic circuits

- Circuits are **equivalent** if the truth tables are the same
 - $a \text{ XOR } b = (a \text{ OR } b) \text{ AND } (a \text{ NAND } b)$
 - $\text{XOR}(a, b) = \text{AND}(\text{OR}(a,b), \text{NAND}(a,b))$



\wedge	0	1
0	0	1
1	1	0

XOR

 


Basic circuits

- Circuits are **equivalent** if the truth tables are the same
 - $a \text{ XOR } b = (a \text{ OR } b) \text{ AND } (a \text{ NAND } b)$
 - $\text{XOR}(a, b) = \text{AND}(\text{OR}(a,b), \text{NAND}(a,b))$



\wedge	0	1
0	0	1
1	1	0

XOR

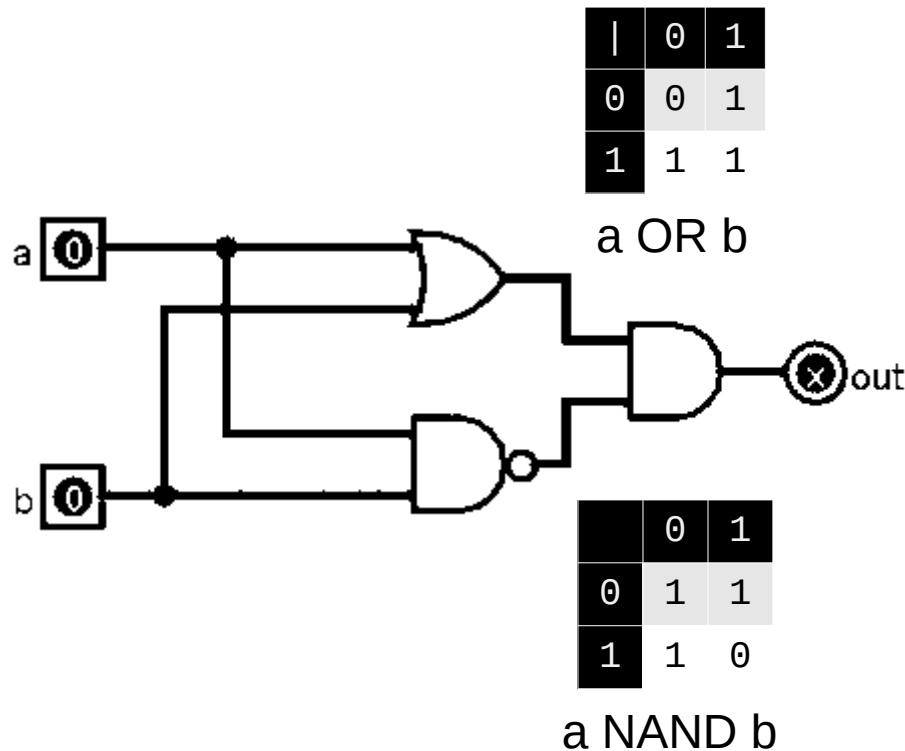

	0	1
0	0	1
1	1	0

(a OR b) AND
(a NAND b)

Basic circuits


- Circuits are **equivalent** if the truth tables are the same
 - $a \text{ XOR } b = (a \text{ OR } b) \text{ AND } (a \text{ NAND } b)$
 - $\text{XOR}(a, b) = \text{AND}(\text{OR}(a,b), \text{NAND}(a,b))$

a	b	$a \wedge b$	$f(a, b)$
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0



\wedge	0	1
0	0	1
1	1	0

XOR

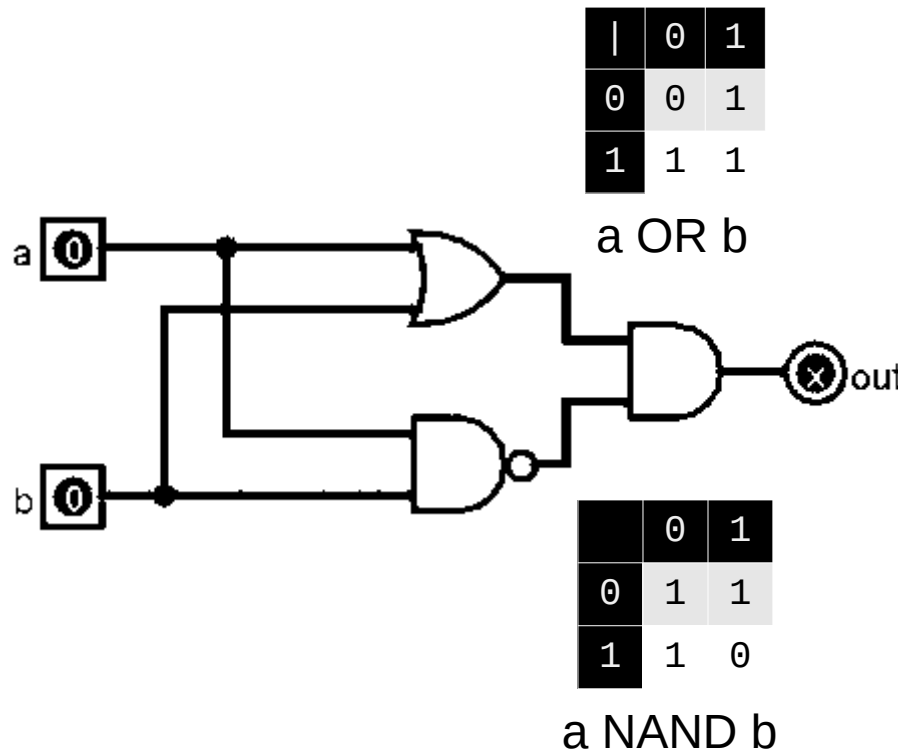

	0	1
0	0	1
1	1	0

$(a \text{ OR } b) \text{ AND } (a \text{ NAND } b)$

$f(a,b)$


Important properties

- Identity: $a \text{ AND } 1 = a$ $(a \text{ OR } 0) = a$
- Constants: $a \text{ AND } 0 = 0$ $(a \text{ OR } 1) = 1$
 - Also: $a \text{ NAND } 0 = 1$ $(a \text{ NOR } 1) = 0$
- Inverses: $a \text{ NAND } 1 = !a$ $(a \text{ NOR } 0) = !a$
 - Also: $a \text{ NAND } a = !a$ $a \text{ NOR } a = !a$
- Double inverse: $!!a = a$
 - Or: $\text{NOT}(\text{NOT}(a)) = a$
- De Morgan's law: $!(a \ \& \ b) = !a \ | \ !b$
 - Alternatively: $!(a \ | \ b) = !a \ \& \ !b$

(remember this from CS 227!)

Universal gates

 - NAND and NOR gates are **universal**
 - Each one alone can reproduce all other gates
 - Example: **a AND b** = $a \& b = \neg(\neg(a \& b)) = \neg(a \text{ NAND } b) = (a \text{ NAND } b) \text{ NAND } (a \text{ NAND } b)$



	0	1
0	1	1
1	1	0

a NAND b

	0	1
0	0	0
1	0	1


(a NAND b) NAND
(a NAND b)

	0	1
0	0	0
1	0	1

a AND b

Universal gates

 - NAND and NOR gates are **universal**
 - Each one alone can reproduce all other gates
 - Example: **a AND b** = $a \& b = \neg(\neg(a \& b)) = \neg(a \text{ NAND } b)$
= **(a NAND b) NAND (a NAND b)**
 - Similarly: **a AND b** = $\neg(\neg(a \& b)) = \neg(\neg a \mid \neg b) = \neg a \text{ NOR } \neg b =$
(a NOR a) NOR (b NOR b)



	0	1
0	1	1
1	1	0

a NAND b


	0	1
0	0	0
1	0	1

(a NAND b) NAND
(a NAND b)



	0	1
0	0	0
1	0	1

a AND b

 

(a NOR a) NOR
(b NOR b)


Circuit types

- Two main kinds of circuits:
 - **Combinational** circuits: outputs are a boolean function of inputs
 - Not time-dependent
 - Used for **computation**
 - **Sequential** circuits: output is dependent on previous outputs
 - Time-dependent
 - Used for **memory**

Computation


- Goal: identify circuits that perform useful computation
 - Testing bits to see if they're equal
 - Selecting between multiple inputs
 - Adding or subtracting bits
 - Bitwise operations (AND, OR, XOR)
 - Make them work on bytes instead of bits

Equality

 


$$a \text{ EQ } b = (a \ \& \ b) \ | \ (!a \ \& \ !b)$$

Multiplexor (“selector”)

 

$$\text{MUX}(a, b, s) = (s \ \& \ a) \ | \ (!s \ \& \ b)$$


Half adders

 

Half Adder

A	B	C	S
0	0	?	?
0	1	?	?
1	0	?	?
1	1	?	?

Half adders

 

Half Adder

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


$$a + b = a \wedge b + a \& b$$

sum carry

Abstraction

- Name circuits, then use them to build more complex circuits
 - E.g., use bit-level EQ to build a word-level equality circuit:

A). Bit-level implementation

 


B). Word-level abstraction




Word-level 2-way multiplexer


A). Bit-level implementation

 

B). Word-level abstraction

 


Word-level 4-way multiplexer

 

How many selector inputs would be required for eight data inputs?


How many data inputs could be supported using four selector inputs?

Full adders

 


Full Adder

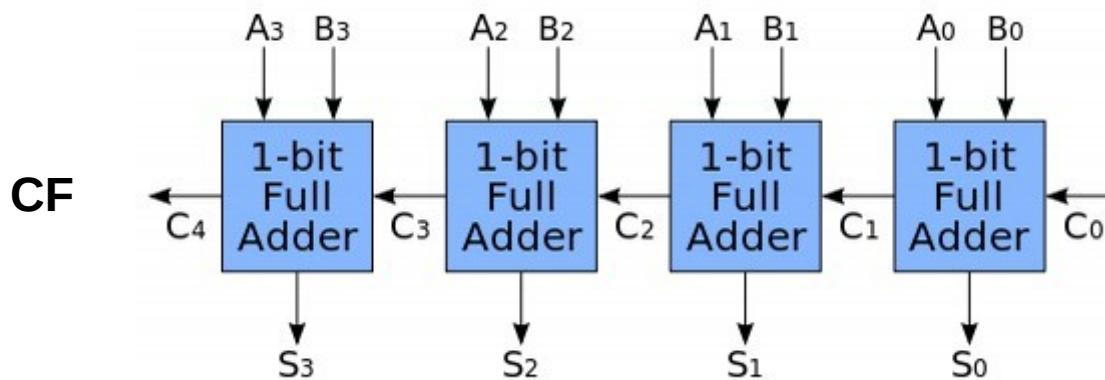Connect full adders to build a **ripple-carry adder** that can handle multi-bit addition:



Adder/subtractor

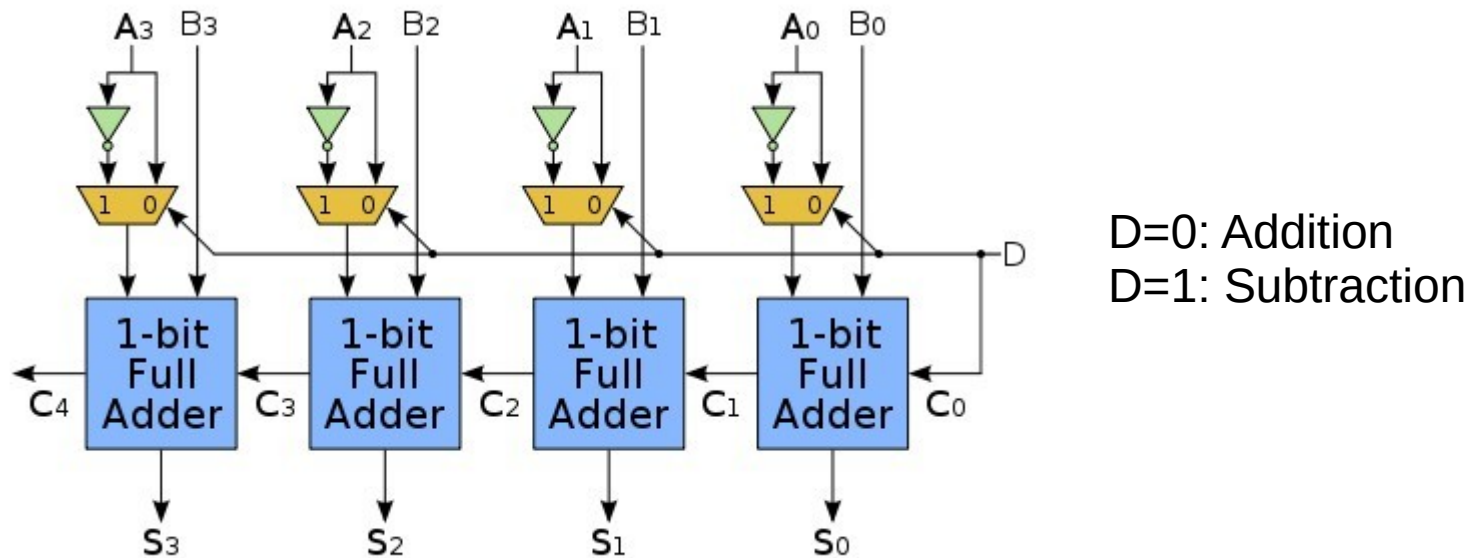


In two's complement: $B - A = B + \sim A + 1$

(invert carry-out for CF if D=1)

ALUs

 
- Combine **adders** and **multiplexors** to make arithmetic/logic units



Basic Arithmetic Logic Unit (ALU)


CPUs

 - Combine **ALU** with **registers** and **memory** to make CPUs



Computers

 - Combine **CPU** with other electronic components and devices (similarly constructed) communicating via **buses** to make a **computer**



Big picture

- Basic systems design approach: exploit **abstraction**
 - Start with simple components
 - Combine to make more complex components
 - Repeat using the new components as **black box** “simple components”
- This is true of most areas in systems
 - **CS 261**: transistors → gates → circuits → adders/flip-flops → ALUs/registers → CPUs/memory → computers
 - **CS 261**: machine code → assembly → C code → Java/Python code
 - **CS 361/470**: threads → processes → nodes → networks/clusters
 - **CS 432**: scanner → parser → analyzer → code generator → optimizer
 - **CS 450**: files + processes + I/O → kernel → operating system
 - **CS 455**: byte stream → frames → packets → datagrams → messages
 - **CS 456**: multiplexers → primitives → modules → CPUs (on FPGAs)

Course status

- We've hit the bottom
 - Or at least as far down as we're going to go (logic gates); from here we go back up!
- Next up:
 - Sequential circuits
 - CPU architecture

Suggestion: download **Logisim** (already installed on lab machines) and play around with some circuits!